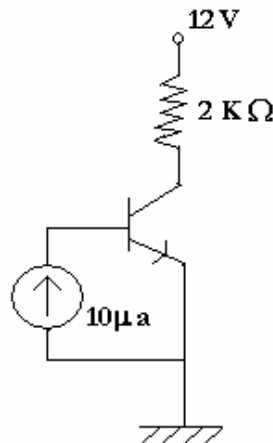


Code No.210551

OR**I-B.Tech I-Semester Supplementary Examinations May/June 2004****ELECTRONICS DEVICES AND CIRCUITS****(Computer Science and Engineering)****Time: 3 hours****Max. Marks: 70****Answer any FIVE questions****All questions carry equal marks**

- 1.a) Explain the construction, operation and applications of the varactor diode.
- b) In a p-type semiconductor, the Fermi level lies 0.4 eV above the valence band. Determine the new position of the Fermi level if the concentration of acceptor atoms is multiplied by a factor of (i) 0.5 and (ii) 4.0. $KT = 0.025\text{eV}$.
- 2.a) Determine the resistivity of germanium (a) in intrinsic condition at 300°K (b) with donor impurity of 1 in 10^7 (c) with acceptor impurity of 1 in 10^8 (d) with both the above impurities simultaneously. Give for germanium at room temperature.
 $\eta_i = 2.5 \times 10^{13} / \text{cm}^3$; $\mu_p = 1800 \text{ cm}^2/\text{V-s}$, $\mu_n = 3800 \text{ cm}^2/\text{V-s}$ and no of germanium atoms/ $\text{cm}^3 = 4.4 \times 10^{22}$.
- b) Explain "Avalanche and zener breakdown."
- 3.a) A silicon transistor with $V_{BE} = 0.7\text{V}$, $\alpha = 0.98$ and collector cut-off current of $10 \mu\text{A}$ is connected as shown. Find (i) β and I_{CO} (ii) I_C , I_E and V_{CE}



- b) Briefly describe some applications of JFET.

Code No.210551

OR

- 4.a) Compare electrostatic and magnetostatic deflection. Why is magnetic deflection preferred to electrostatic deflection in CRT used in TV?
- b) In a CRT having electric deflection system, the deflection plates are 2cm. long and having a uniform spacing of 4mm between them. The fluorescent screen is 25cm away from the centre of the deflection plates. Calculate (i) deflection sensitivity (ii) velocity of electron on reaching the field (ii) deflection produced on the screen.
- 5.a) Consider the filter shown. Determine (i) the filter transfer function V_2/V_1 and therefrom the output voltage for an input voltage of

$$v(t) = \frac{200\sqrt{2}}{\pi} \left[1 - \frac{4}{3} \cos 62\delta t \right]$$

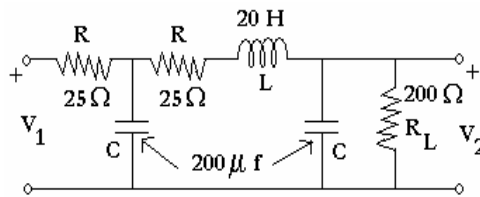


fig.

Wherein harmonics higher than second are ignored.

(ii) ripple factor $R = 25\Omega$, $R_L = 200\Omega$, $C = 200\mu f$, $L = 20H$.

- b) Can the value of stability factor be less than unity ? Explain .
- 6.a) Discuss the effect of coupling capacitor on low frequency response.
- b) For the amplifier shown compute input and output impedances and individual and over all voltage and current gains using approximate analysis.

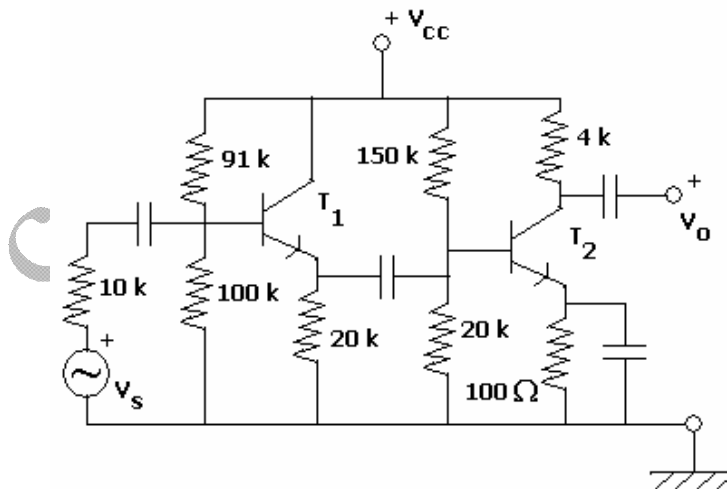


Fig.

For Online Notes Visit us at

<http://www.campusexpress.co.in>

Code No.210551

OR

- 7.a) Define the condition for thermal stability.
 - b) Draw a neat diagram of a CRT and explain.
8. Write short notes on
- (a) Photo Transistor
 - (b) Monolithic Ic
 - (c) Depletion MOSFET